

The logic of computers

starting in **5:00**

"To be, or not to be ..."

- Shakespeare



Dr. Goran Soldar
Dr. Khuong An Nguyen



Boolean algebra



Combinational circuit



Sequential circuit

1

Boolean algebra.

2

Combinational circuit.

3

Sequential circuit.




Boolean
algebra

Boolean algebra

1 Algebra on 0 and 1.

2 Has its root in philosophy.

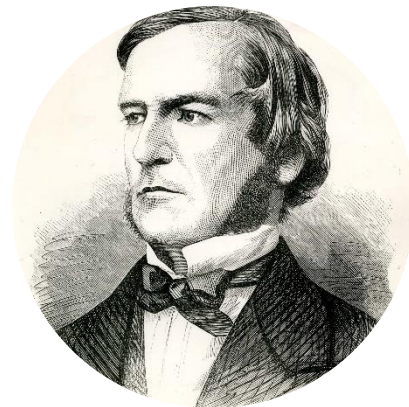

1. What we start

Axioms: assuming basic objects and operations are true.

2. What we derive

Laws and theorems: manipulating Boolean expressions

3. What we build

Circuit: deriving complex digital design.

Further reading

“The Mathematical analysis of Logic”. George Boole, 1847



Combinational
logic



Sequential
logic



Boolean
algebra







Combinational
logic



Sequential
logic

Ordinary vs Boolean algebra
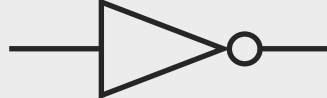
| | Ordinary algebra | Boolean algebra |
|-----------|---|---|
| Inputs | 1 | false 0 |
| Operators | <div><div>+</div><div>-</div><div>x</div><div>÷</div></div> | <div><div> AND</div><div> OR</div><div> NOT</div><div> XOR</div></div> |



Boolean
algebra

AND operation

Symbol



Boolean Expression

Given Input #1 = A; Input #2 = B; Output = Q

$$Q = A \bullet B$$

Truth table

| Input #1 | Input #2 | Output |
|-----------|-----------|-----------|
| True (1) | True (1) | True (1) |
| True (1) | False (0) | False (0) |
| False (0) | True (1) | False (0) |
| False (0) | False (0) | False (0) |



Combinational
logic




Sequential
logic



Boolean
algebra

OR operation

Symbol

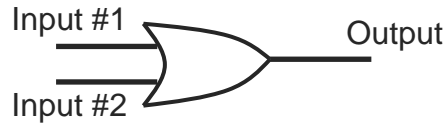


Boolean Expression

Given Input #1 = A; Input #2 = B; Output = Q

$$Q = A + B$$

Truth table

| Input #1 | Input #2 | Output |
|-----------|-----------|-----------|
| True (1) | True (1) | True (1) |
| True (1) | False (0) | True (1) |
| False (0) | True (1) | True (1) |
| False (0) | False (0) | False (0) |

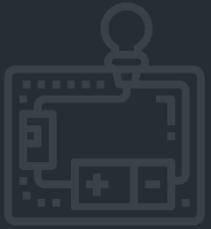

Combinational
logic



Sequential
logic



Boolean
algebra




Combinational
logic



Sequential
logic

NOT operation

Symbol

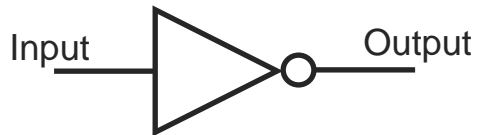

Expression

Given Input = A; Output = Q

$$Q = \bar{A}$$

Truth table

| Input | Output |
|-----------|-----------|
| True (1) | False (0) |
| False (0) | True (1) |



Boolean
algebra




Combinational
logic



Sequential
logic

XOR (Exclusive-OR) operation

Symbol

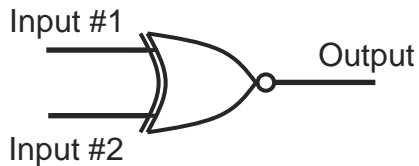

Boolean Expression

Given Input #1 = A; Input #2 = B; Output = Q


$$Q = A \oplus B = \bar{A} B + A \bar{B}$$

Truth table

| Input #1 | Input #2 | Output |
|-----------|-----------|-----------|
| True (1) | True (1) | False (0) |
| True (1) | False (0) | True (1) |
| False (0) | True (1) | True (1) |
| False (0) | False (0) | False (0) |



Boolean
algebra


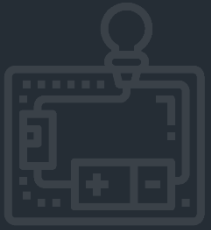


Combinational
logic



Sequential
logic

Designing a circuit

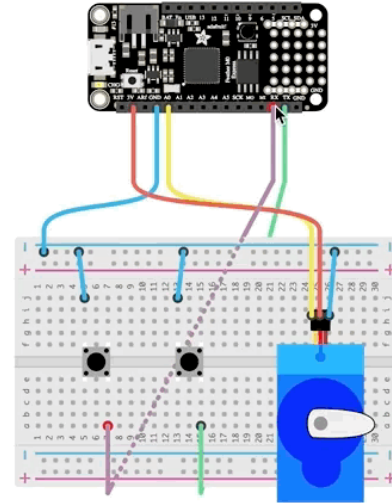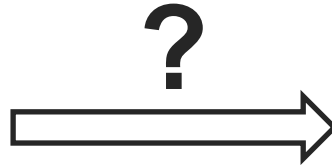



Boolean
algebra

Truth table

- 1 Lists all possible inputs and outputs.
- 2 Two circuits are identical, if they share the same truth table.

AND operator



Truth table

| Input #1 | Input #2 | Output |
|-----------|-----------|-----------|
| True (1) | True (1) | True (1) |
| True (1) | False (0) | False (0) |
| False (0) | True (1) | False (0) |
| False (0) | False (0) | False (0) |



Combinational
logic



Sequential
logic



Boolean
algebra

Step 1: Writing the truth table

Specification:

A circuit that accepts 3 inputs, and returns True, only when one input is False.

Writing the truth table:

A circuit with n inputs will always have 2^n rows (possibilities).

Truth table

| Input A | Input B | Input C | Output |
|-----------|-----------|-----------|-----------|
| True (1) | True (1) | True (1) | False (0) |
| True (1) | True (1) | False (0) | True (1) |
| True (1) | False (0) | True (1) | True (1) |
| True (1) | False (0) | False (0) | False (0) |
| False (0) | True (1) | True (1) | True (1) |
| False (0) | True (1) | False (0) | False (0) |
| False (0) | False (0) | True (1) | False (0) |
| False (0) | False (0) | False (0) | False (0) |



Combinational
logic



Sequential
logic



Boolean
algebra

Step 2: Deriving Boolean expressions

1 Find all rows with output True (1).

For each row:

2 if the input X is 1, write X
if the input X is 0, write \bar{X}

Truth table

| Input A | Input B | Input C | Output | Expression |
|-----------|-----------|-----------|-----------|---------------------------|
| True (1) | True (1) | True (1) | False (0) | |
| True (1) | True (1) | False (0) | True (1) | $A \cdot B \cdot \bar{C}$ |
| True (1) | False (0) | True (1) | True (1) | $A \cdot \bar{B} \cdot C$ |
| True (1) | False (0) | False (0) | False (0) | |
| False (0) | True (1) | True (1) | True (1) | $\bar{A} \cdot B \cdot C$ |
| False (0) | True (1) | False (0) | False (0) | |
| False (0) | False (0) | True (1) | False (0) | |
| False (0) | False (0) | False (0) | False (0) | |




Combinational
logic



Sequential
logic



Boolean
algebra

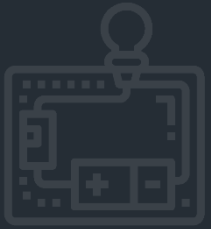

Combinational
logic



Sequential
logic

Step 3: Sum of the products

OR (+) all the product of the rows together.

$$A \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot C$$

Truth table

| Input A | Input B | Input C | Output | Expression |
|-----------|-----------|-----------|-----------|---------------------------|
| True (1) | True (1) | True (1) | False (0) | |
| True (1) | True (1) | False (0) | True (1) | $A \cdot B \cdot \bar{C}$ |
| True (1) | False (0) | True (1) | True (1) | $A \cdot \bar{B} \cdot C$ |
| True (1) | False (0) | False (0) | False (0) | |
| False (0) | True (1) | True (1) | True (1) | $\bar{A} \cdot B \cdot C$ |
| False (0) | True (1) | False (0) | False (0) | |
| False (0) | False (0) | True (1) | False (0) | |
| False (0) | False (0) | False (0) | False (0) | |



Boolean
algebra



Combinational
logic



Sequential
logic

Expression simplification

Axioms

- Closure, given $a, b \in B$:
 $a + b \in B$
 $a \bullet b \in B$
- Commutative, given $a, b \in B$
 $a + b = b + a$
 $a \bullet b = b \bullet a$
- Identity, given $0, 1 \in B$:
 $a + 0 = a$
 $a \bullet 1 = a$
- Distributive :
 $a + (b \bullet c) = (a + b) \bullet (a + c)$
 $a \bullet (b + c) = a \bullet b + a \bullet c$
- Complement :
 $a + \bar{a} = 1$
 $a \bullet \bar{a} = 0$



Laws

- Operation with 0 and 1 :
 $X + 0 = X$ $X \bullet 1 = X$
 $X + 1 = 1$ $X \bullet 0 = 0$
- Idempotent :
 $X + X = X$ $X \bullet X = X$
- Involution :
 $\overline{(\bar{X})} = X$
- Complementarity :
 $X + \bar{X} = 1$ $X \bullet \bar{X} = 0$
- Commutative :
 $X + Y = Y + X$ $X \bullet Y = Y \bullet X$
- Associative :
 $(X + Y) + Z = X + (Y + Z)$
 $(X \bullet Y) \bullet Z = X \bullet (Y \bullet Z)$
- Distributive :
 $X \bullet (Y + Z) = (X \bullet Y) + (X \bullet Z)$
 $X + (Y \bullet Z) = (X + Y) \bullet (X + Z)$



Boolean
algebra

Circuit design steps

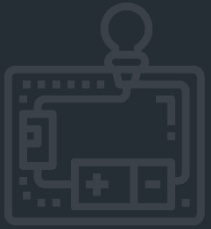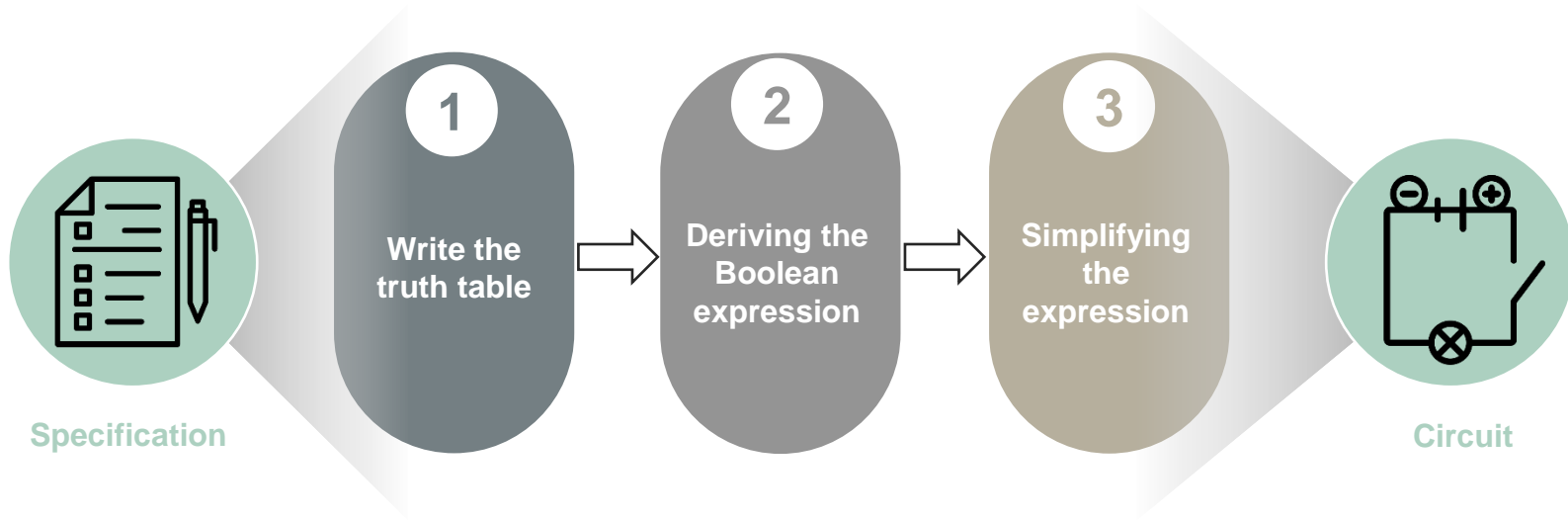


Combinational
logic




Sequential
logic

Signal delay

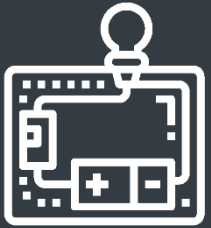- 1 We often assume the signal output happens immediately.
- 2 CPU speed limitation: cannot perform more calculations per second than its capability.



Combinational
logic

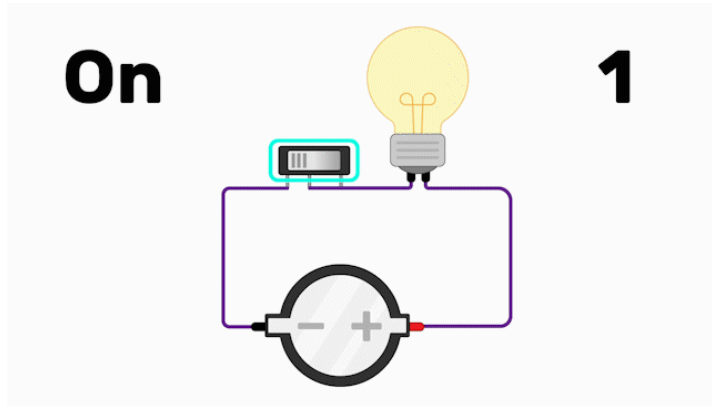


Sequential
logic

Electronic signal (in theory)





Boolean
algebra

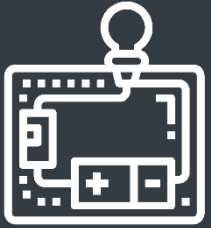

Combinational
logic




Sequential
logic

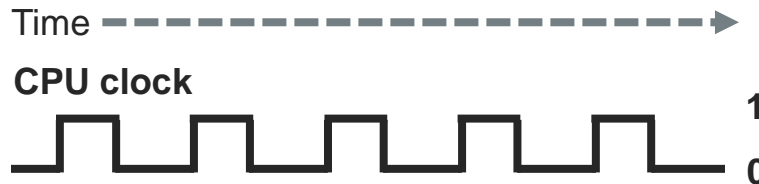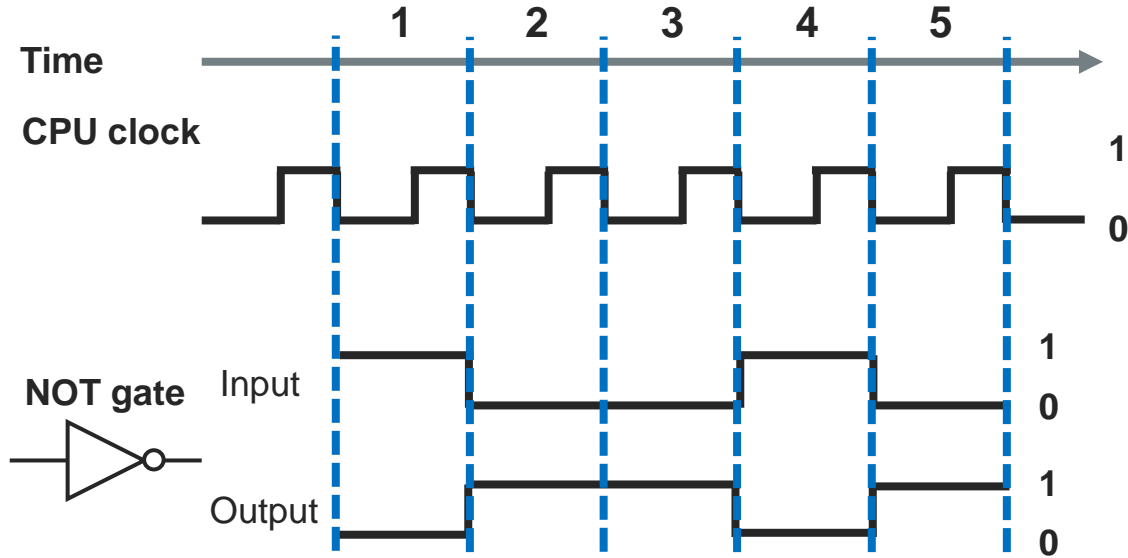


= 1 clock cycle

Electronic signal (in reality)

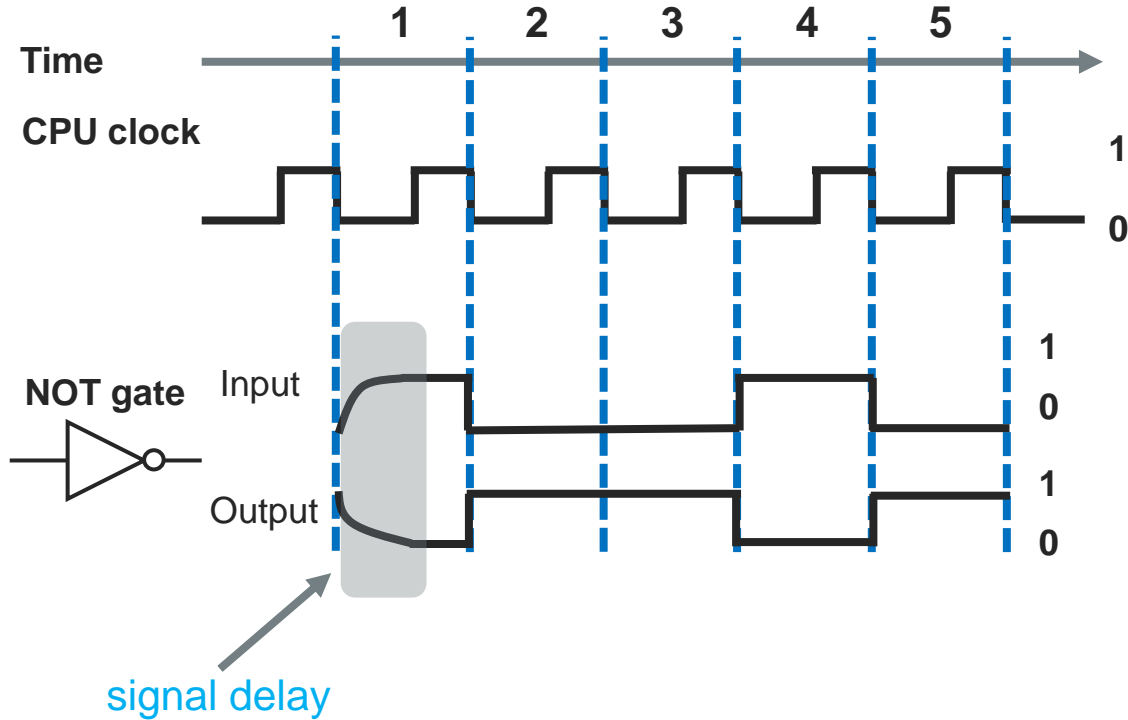

Boolean
algebra

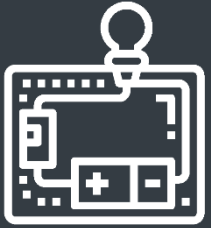



Combinational
logic



Sequential
logic

Processing delay

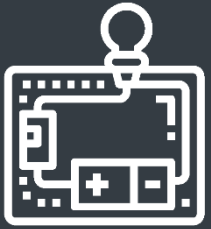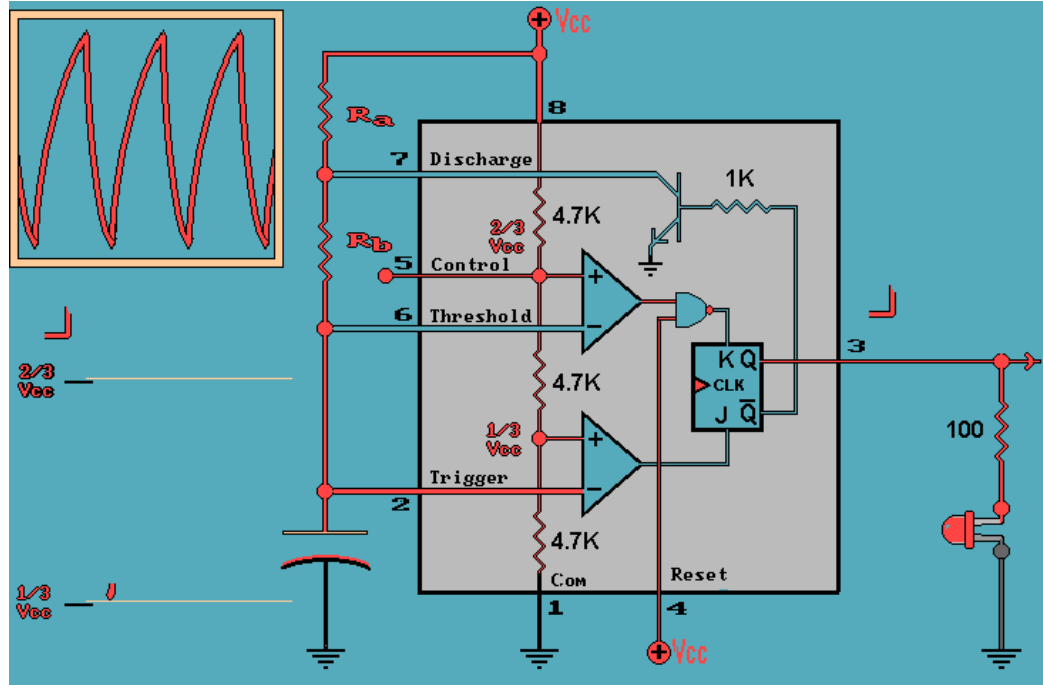Complex circuit takes time to process the inputs.




Combinational
logic



Sequential
logic

Combinational logic

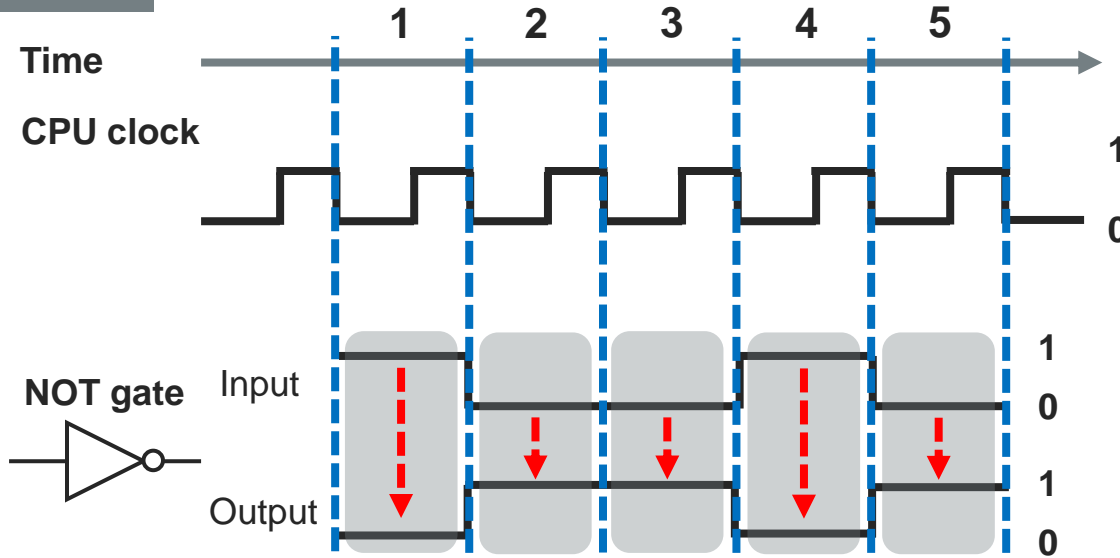

AND gate




OR gate



XOR gate



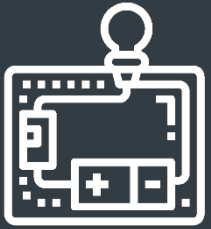- 1 Takes some inputs, and produces some outputs.
- 2 All processing happens within one time unit.
- 3 $\text{output}[t] = \text{function}(\text{input}[t])$.



Combinational logic




Sequential logic


Sequential logic




Boolean
algebra

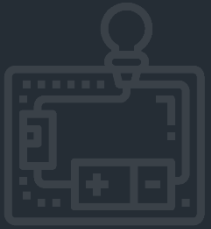

Combinational
logic

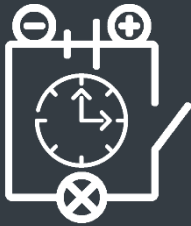


Sequential
logic

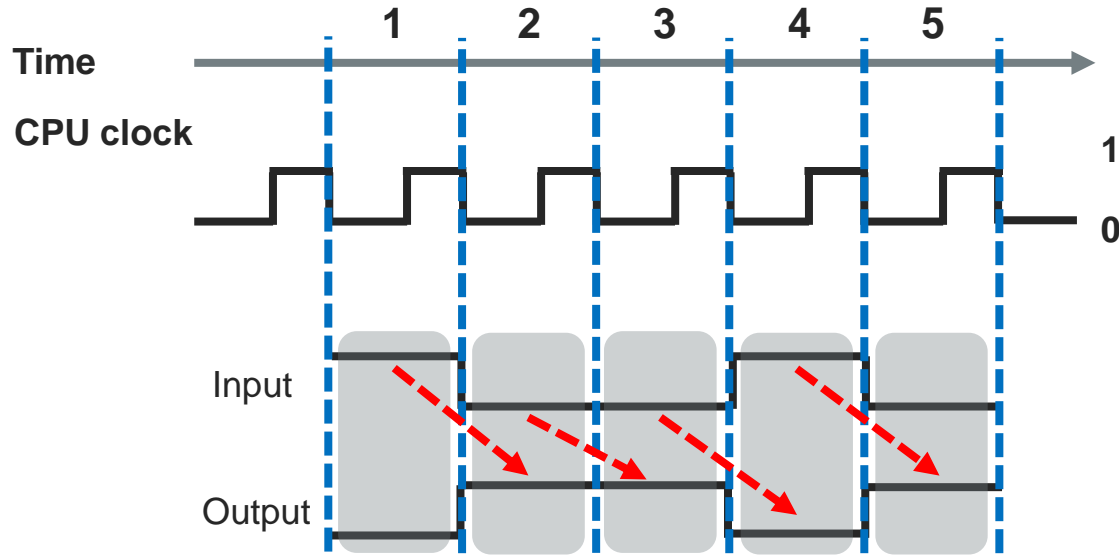

Output depends on the input, and the previous states
$$\text{output}[t] = \text{function}(\text{input}[t - 1]).$$

S-R Flip-Flop

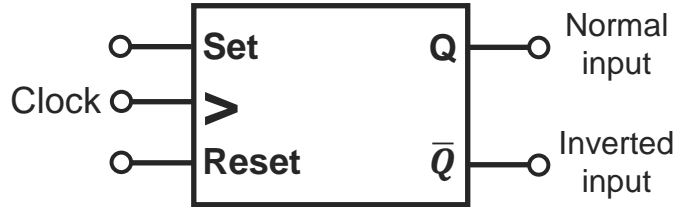

Set state

$$Q = 1$$

$$\bar{Q} = 0$$

Reset state

$$Q = 0$$

$$\bar{Q} = 1$$


1 1-bit storage device.

2 Output can be set to store 0 or 1, depending on the inputs.


3 Flip-Flop retains its outputs, even without input signals.



Boolean
algebra


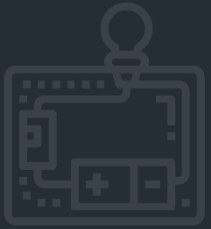


Combinational
logic

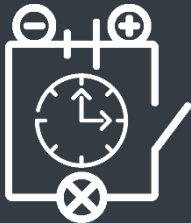

Sequential
logic

S-R Flip-Flop

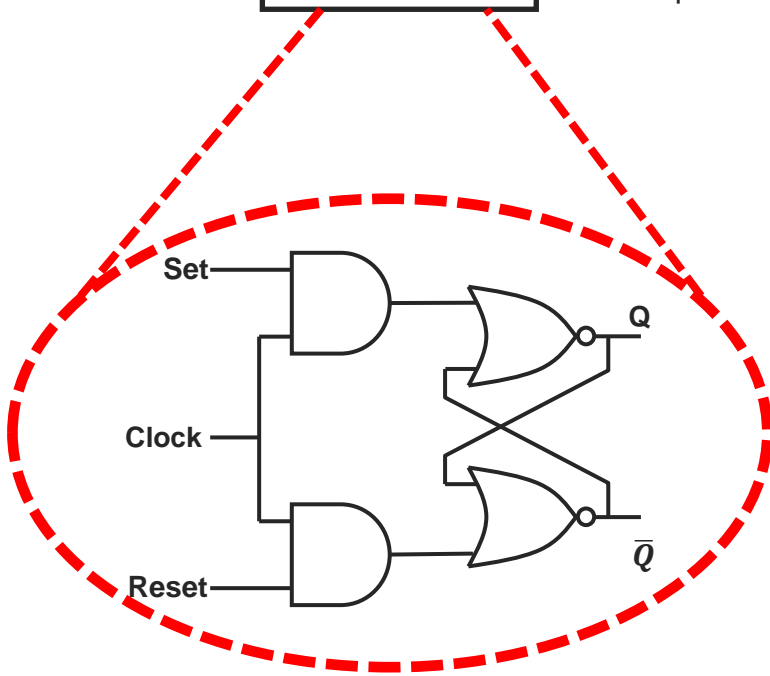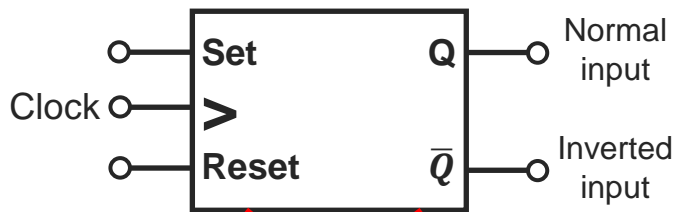

Truth table

| Set | Reset | Q | \bar{Q} |
|-----|-------|-----------|-----------|
| 0 | 0 | no change | |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | invalid | |



Boolean
algebra




Combinational
logic



Sequential
logic

J-K Flip-Flop

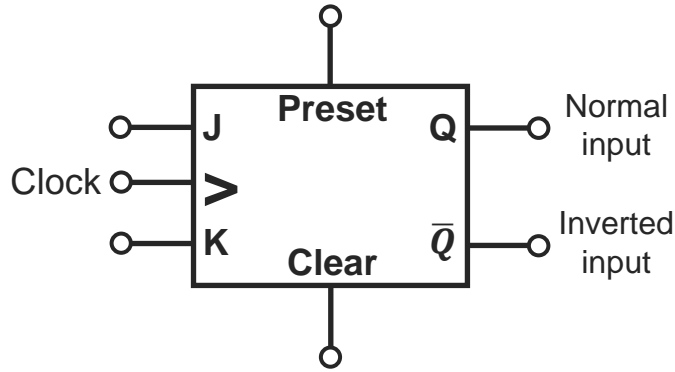


Truth table

| J | K | Q | \bar{Q} |
|---|---|-----------|-----------|
| 0 | 0 | no change | |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | toggle | |

- 1 An improvement over S-R Flip-Flop.
- 2 No invalid state.
- 3 When $J = K = 1$, the output toggles between 0 and 1.



Boolean
algebra

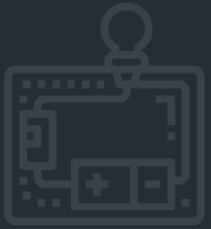

Combinational
logic




Sequential
logic

Traffic light example




Boolean
algebra

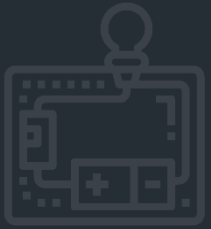

Combinational
logic



Sequential
logic

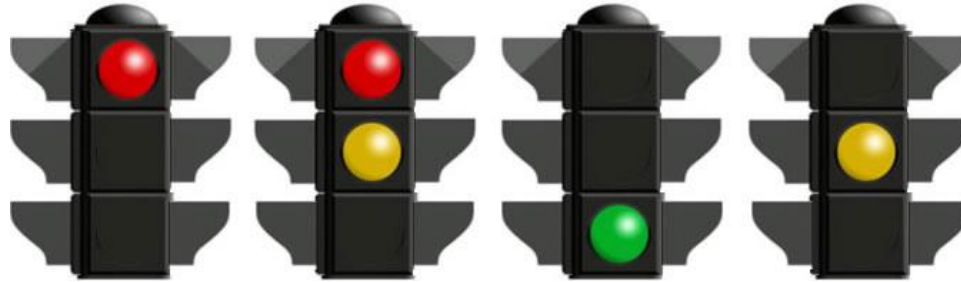

RED

RED
AMBER

GREEN

AMBER



Questions, feedback



Cockcroft building
C519 (Khuong)
C537 (Goran)



K.A.Nguyen@brighton.ac.uk
G.Soldar@brighton.ac.uk



<https://khuong.uk>



(SMBC comic)